

# Typical stages in digital signal processing

## A/D Conversion

Dr. Ing. Rodrigo Gonzalez

`rodralez@frm.utn.edu.ar`

`rodrigo.gonzalez@ingenieria.uncuyo.edu.ar`




**UNCUYO**  
UNIVERSIDAD  
NACIONAL DE CUYO

- 1 A/D Conversion Stages
- 2 Quantizer
- 3 ADC Signal-to-Noise relationship
- 4 ADC resolution for a particular signal
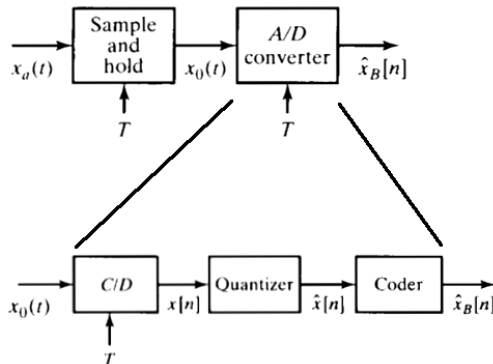
# A/D Conversion Stages

- The A/D converter is a physical device that converts a voltage or current amplitude at its input into a binary code representing a quantized amplitude value closest to the amplitude of the input.
- The sample-and-hold stage can be a **zero-order-hold**.



# Quantizer

- Uniformly spaced quantizer, function  $Q(x)$ .
- The number of quantization levels will be a power of two ( $2^B$ ).
- Precision of quantizer,  $\Delta = \frac{\text{full voltage range}}{2^{\text{word length}}} = \frac{2V_p}{2^B} \cdot [mV]$

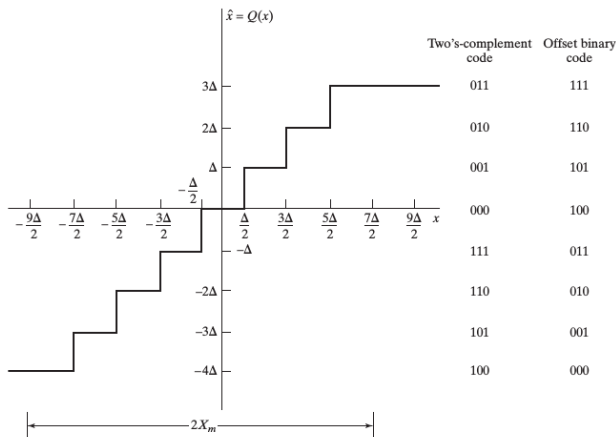


Figure 4.54 Typical quantizer for A/D conversion.

# Quantizer Error example



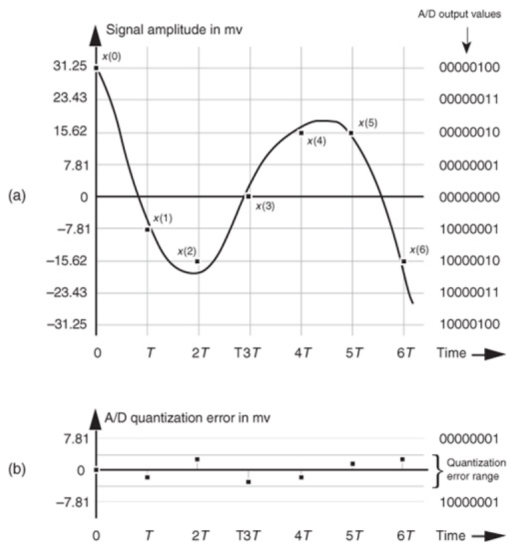


Figure: 12.1 [2]

## Quantizer Error example, II

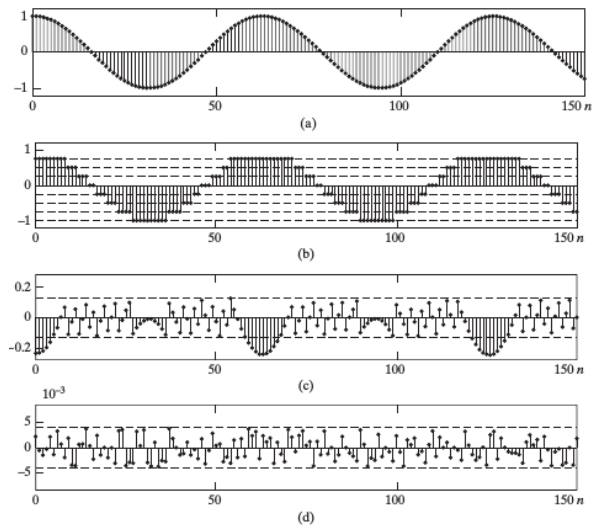

**Figure 4.57** (continued) (b) Quantized samples of the cosine waveform in part (a) with a 3-bit quantizer. (c) Quantization error sequence for 3-bit quantization of the signal in (a). (d) Quantization error sequence for 8-bit quantization of the signal in (a).

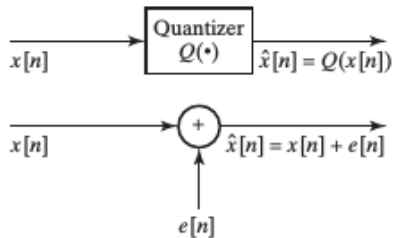

**Figure 4.56** Additive noise model for quantizer.

The precision of the quantizer is given by [2]:

$$\Delta = q = \frac{\text{full voltage range}}{2^{\text{word length}}} = \frac{2V_p}{2^B} \cdot [mV] \quad (1)$$


- $SNR = (P_{\text{signal}})/(P_{\text{noise}})$  relates two powers.
- Since  $q$  is defined as a random variable, its power cannot be represented explicitly.
- A statistical version of SNR is used,

$$SNR_{ADC} = 10 \cdot \log_{10} \left( \frac{\text{input signal variance}}{\text{A/D quantization noise variance}} \right), \quad [\text{dB}] \quad (2)$$

$$= 10 \cdot \log_{10} \left( \frac{\sigma_{\text{signal}}^2}{\sigma_{ADC}^2} \right). \quad (3)$$



# ADC Signal-to-Noise relationship, II

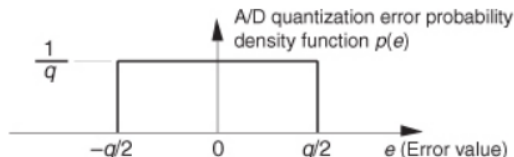

$$\sigma_{ADC}^2 = \int_{-q/2}^{q/2} (e - \mu)^2 p(e) de = \int_{-q/2}^{q/2} e^2 p(e) de = \frac{1}{q} \int_{-q/2}^{q/2} e^2 de = \frac{q^2}{12}, \quad (4)$$

$$\sigma_{ADC}^2 = \left( \frac{2V_p}{2^B} \right)^2 \cdot \frac{1}{12} = \boxed{\frac{V_p^2}{3 \cdot 2^{2B}}}, \quad (5)$$

$$\text{Load Factor, } LF = \frac{rms_{signal}}{V_p} = \frac{\sigma_{signal}}{V_p} \Rightarrow \sigma_{signal}^2 = \boxed{LF^2 \cdot V_p^2}, \quad (6)$$

$$\begin{aligned} SNR_{ADC} &= 10 \cdot \log_{10} \left( \frac{\sigma_{signal}^2}{\sigma_{ADC}^2} \right), \\ &= 10 \cdot \log_{10} \left[ \left( LF^2 \cdot V_p^2 \right) \cdot \frac{3 \cdot 2^{2B}}{V_p^2} \right] = 10 \cdot \log_{10} \left[ \left( LF^2 \cdot 3 \cdot 2^{2B} \right) \right], \end{aligned} \quad (7)$$

$$= 10 \cdot \left[ \log_{10}(LF^2) + \log_{10}(3) + 2 \log_{10}(2) \cdot B \right], \quad (8)$$

$$= 20 \cdot \log_{10}(LF) + 4.77 + 6.02 \cdot B. \quad [\text{dB}] \quad (9)$$

# ADC Signal-to-Noise relationship considerations

$$\begin{aligned} SNR_{ADC} &= 20 \cdot \log_{10}(LF) + 4.77 + 6.02 \cdot B, \quad [\text{dB}] \\ &= 20 \cdot \log_{10}\left(\frac{rms_{signal}}{V_p}\right) + 4.77 + 6.02 \cdot B. \quad [\text{dB}] \end{aligned}$$

Considerations about  $LF$ :

- Ideally, if  $rms_{signal} \gg V_p$ ,  $SNR_{ADC}$  **increases**, but this will produce a severe distortion in the sampling signal (saturation).
- On the other hand, if  $rms_{signal} \ll V_p$ ,  $SNR_{ADC}$  **decreases**.

Considerations about  $B$  (numbers of bits):

- $SNR_{ADC}$  increases 6 dB by each bit in ADC's quantizer.
- So, the more bits the better, isn't it?

Other sources of error should be taken into account:

- It was considered that ADC's  $V_{MAX} = V_p$ .
- The proposed model for the probability density function of  $e[n]$  may not be uniform.
- Therefore,  $SNR_{ADC}$  from Eq. 9 should be **decreased by 3 or 6 dB**.

For a sinusoidal signal,  $rms_{signal} = V_p/\sqrt{2}$ .

$$SNR_{ADC} = 20 \cdot \log_{10} \left( \frac{rms_{signal}}{V_p} \right) + 4.77 + 6.02 \cdot B, \quad (10)$$

$$= 20 \cdot \log_{10} \left( \frac{V_p/\sqrt{2}}{V_p} \right) + 4.77 + 6.02 \cdot B. \quad (11)$$

Thus, the maximum  $SNR_{ADC}$  is,

$$SNR_{ADC} = 20 \cdot \log_{10} \left( 1/\sqrt{2} \right) + 4.77 + 6.02 \cdot B, \quad (12)$$

$$= -3.01 + 4.77 + 6.02 \cdot B, \quad (13)$$

$$= 1.76 + 6.02 \cdot B. \text{ [dB]} \quad (14)$$

# ADC resolution for a particular signal

Consider the following example:

- The SNR for an audio output amplifier is 110 dB.
- A 24-bits ADC is chosen to sample the output amplifier (professional audio).
- The amplifier is excited by an input sinusoidal signal.

$$SNR_{ADC} = 1.76 + 6.02 \cdot 24 - 3 = 143.24 \text{ dB}.$$

- How many bits are used to measure noise?  $(143 - 110)/6 \simeq 5.5$  bits!.
- In a control loop, picking a bad ADC resolution could lead to a catastrophic scenario.
- What happens if  $B = 10$  bits?  $SNR_{ADC} = 61.96$  dB,  $(110 - 61.96)/6 \simeq 8$  extra bits are needed!.

*Summary: the number of bits  $B$  in an ADC must provide  $SNR_{ADC} \geq SNR_{signal}$ .*

- Rule of thumb: the ADC resolution should be choose in order to provide 6 dB (1 bit) above the SNR of the signal to be sample.
- Additional bits (noisy bits) can be eliminated by right shifting.

In C: `adc_read >>= 5.`

- 1 Alan V. Oppenheim and Ronald W. Schaffer. *Discrete-time signal processing, 3rd Ed.* Prentice Hall. 2010. Section 4.8.
- 2 Richard G. Lyons. *Understanding Digital Signal Processing, 3rd Ed.* Prentice Hill. 2010. Section 12.3.1.
- 3 Paolo Prandoni and Martin Vetterli. *Signal processing for communications.* Taylor and Francis Group, LLC. 2008. Section 9.6.